

Trans-Resistance Amplifier

Sudeep Veggalam*

CONTENTS

For the feedback transresistance amplifier in Fig. , use small-signal analysis to find the open-loop gain G , the feedback H , and the closed loop gain G_m . Neglect r_o of each of the transistors and assume $R_C \ll \beta_2 R_E$ and $R_E \ll R_F$, and that the feedback causes the signal voltage at the input node to be nearly zero. Evaluate $\frac{V_o}{I_s}$ for the following component values: $\beta_1 = \beta_2 = 100$, $R_C = R_E = 10k\Omega$ and $R_F = 100k\Omega$.

1. Draw the small-signal equivalent of the circuit in Fig.1.

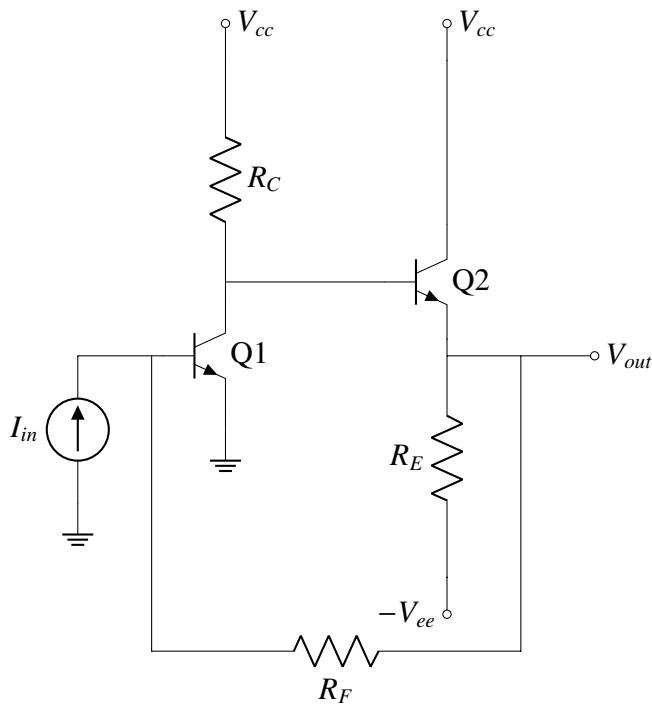


Fig. 1

Solution:

The equivalent circuit is Fig.1

2. Find the expression for the open loop Gain(G) of the system.

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

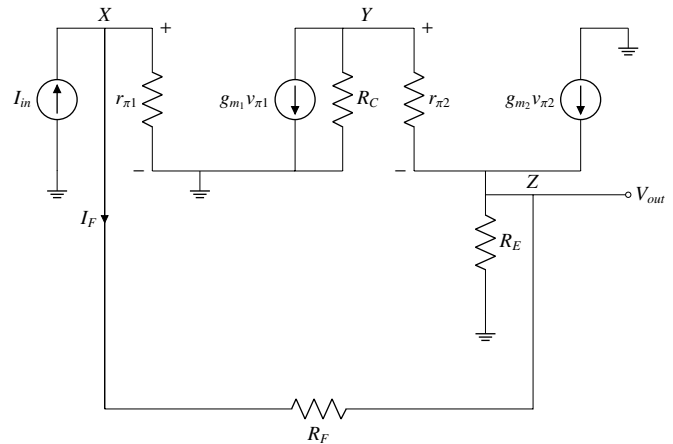


Fig. 1

Solution:

The given system is a cascaded system of Q_1 and Q_2 . The signal flow graph is illustrated in Fig. 2

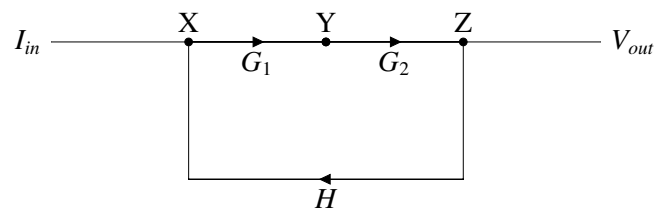


Fig. 2

So, if the gain of Q_1 and Q_2 are G_1 and G_2 respectively, the open-loop gain (G) is given by:

$$G = G_1 G_2 \quad (2.1)$$

Q_1 is in CE(Common-emitter) stage. The input signal is I_{in} . From fig. 1,

$$I_X = I_{in} \quad (2.2)$$

$$\beta = \frac{I_c}{I_b} \quad (2.3)$$

Applying Kirchoff's Law in the loop connect-

ing Y to ground,

$$\Rightarrow V_Y = \beta I_{in} R_C \quad (2.4)$$

$$G_1 = \frac{V_{out}}{I_{in}} = \frac{V_Y}{I_X} \quad (2.5)$$

$$= \beta R_C \quad (2.6)$$

Q_2 is in emitter follower topology.

$$V_{\pi 2} = V_Y - V_Z \quad (2.7)$$

Applying Kirchoff's Law,

$$\frac{V_Y - V_Z}{r_\pi} + g_{m2}(V_Y - V_Z) = \frac{V_Z}{R_E} \quad (2.8)$$

$$\Rightarrow \frac{V_Z}{V_Y} = \frac{R_E}{\frac{1}{g_{m2}} + R_E} \quad (2.9)$$

$$\Rightarrow G_2 = \frac{R_E}{\frac{1}{g_{m2}} + R_E} \quad (2.10)$$

From (2.1), the open loop gain (G):

$$G = (\beta_1 R_C) \left(\frac{R_E}{\frac{1}{g_{m2}} + R_E} \right) \quad (2.11)$$

3. Find the feedback factor(H) of the given circuit.

Solution:

From Fig.1, the feedback circuit consists of only a resistor R_F :

$$\therefore H = \frac{I_F}{V_{out}} = \frac{1}{R_F} \quad (3.1)$$

4. Find the closed loop gain of the system.

Solution:

The closed loop gain of a system is given by:

$$G_L = \frac{G}{1 + GH} \quad (4.1)$$

From (2.11) and (3.1). The closed loop gain of the circuit is given by:

$$G_L = \frac{(\beta_1 R_C) \left(\frac{R_E}{\frac{1}{g_{m2}} + R_E} \right)}{1 + \frac{(\beta_1 R_C) \left(\frac{R_E}{\frac{1}{g_{m2}} + R_E} \right)}{R_F}} \quad (4.2)$$

$$= \frac{R_F R_C R_E \beta}{\beta R_C R_E + R_F \left(\frac{1}{g_{m2}} + R_E \right)} \quad (4.3)$$

5. Find G, H and G_L for the given problem. Parameters are summarised in table 5.

Parameters	Value
V_{cc}	5V
β_1	100
β_2	100
R_C	10K Ω
R_E	10K Ω
R_F	100K Ω

TABLE 5

Solution:

To calculate the bias values of Q1, Q2. Remove the input and output, the resultant circuit is shown in fig.5

Applying KVL to the circuit, we get:

$$0.7 + I_{b1} R_F + (I_{b1} - (\beta + 1) I_{b2}) R_E = -V_{ee} \quad (5.1)$$

$$0.7 + I_{b1} R_F + 0.7 + (\beta I_{b1} + I_{b2}) R_C = V_{cc} \quad (5.2)$$

Solving the above equations, we get:

$$I_{b1} = \frac{\frac{V_{cc}-1.4}{R_C} - \frac{V_{ee}+0.7}{R_E(\beta+1)}}{\frac{R_F+\beta R_C}{R_C} + \frac{R_E+R_F}{R_E(\beta+1)}} \quad (5.3)$$

$$= 3.22 * 10^{-6} \quad (5.4)$$

$$I_{b2} = \frac{\frac{V_{cc}-1.4}{\beta R_C + R_F} + \frac{V_{ee}+0.7}{R_E+R_F}}{\frac{R_C}{R_F+\beta R_C} + \frac{R_E(\beta+1)}{R_E+R_F}} \quad (5.5)$$

we know,

$$g_m = \frac{I_c}{V_T} \quad (5.6)$$

where, $V_T = 26\text{mV}$, and

$$r_\pi = \frac{\beta}{g_m} \quad (5.7)$$

$$\therefore g_{m1} = \frac{\beta I_{b1}}{V_T} \quad (5.8)$$

$$= 0.0123 \quad (5.9)$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} \quad (5.10)$$

$$= 8130\Omega \quad (5.11)$$

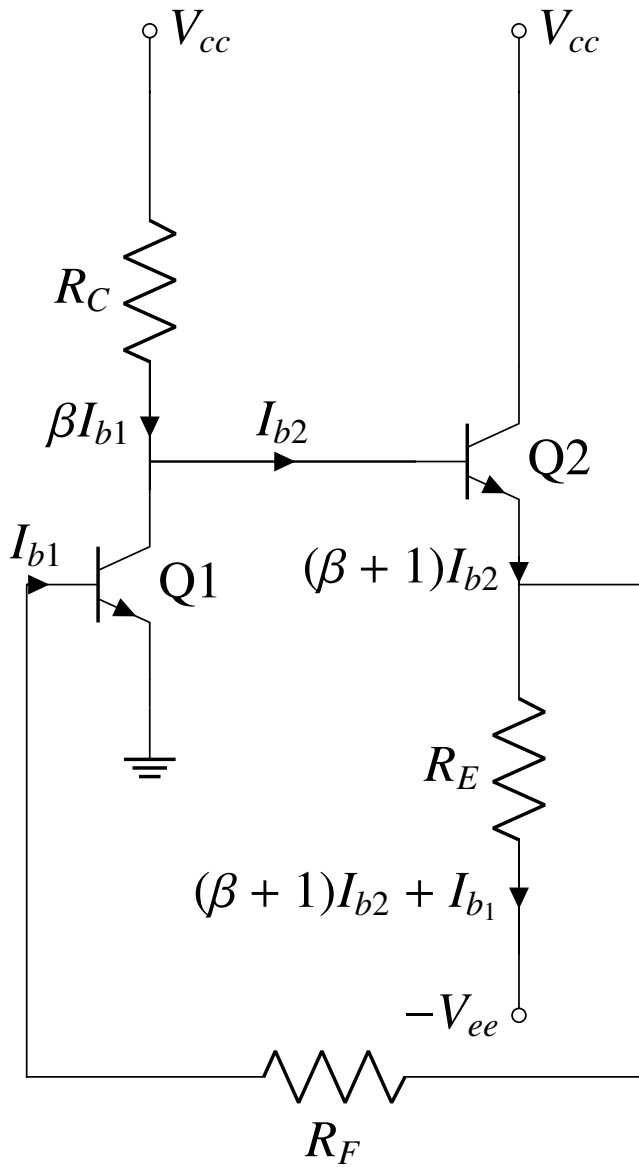


Fig. 5

$$\therefore g_{m2} = \frac{\beta I_{b2}}{V_T} \quad (5.12)$$

$$= 0.023 \quad (5.13)$$

$$r_{\pi 2} = \frac{\beta}{g_{m2}} \quad (5.14)$$

$$= 4347.8\Omega \quad (5.15)$$

From (2.11), the open loop gain (G):

$$G = (100 * (10K)) \left(\frac{10^4}{10^4 + \frac{1}{0.023}} \right) \Omega \quad (5.16)$$

$$= (10^6) (0.995) \quad (5.17)$$

$$= 995670\Omega \quad (5.18)$$

From (3.1), the feedback (H):

$$H = \frac{1}{100K} \Omega^{-1} \Rightarrow H = 10^{-5} \Omega^{-1} \quad (5.19)$$

From (4.3), the closed loop gain (G_L):

$$G_L = \frac{995670}{1 + (995670)(10^{-5})} \Omega \quad (5.20)$$

$$= 99006.52\Omega \quad (5.21)$$

6. Verify the result using spice simulation.

Solution:

The following netlist simulates the closed loop gain for a sinusoidal signal of amplitude 10^{-6}

```
codes/ee18btech11045/spice/
ee18btech11045_clresult.net
```

The output is plotted using the following code.

```
codes/ee18btech11045/spice/
ee18btech11045_clresult.py
```

The output is plotted in fig. 6. The output amplitude is shown to be 0.1 .

$$\therefore \frac{V_{out}}{I_{in}} \approx 10^5 \quad (6.1)$$

This proves the value calculated in (5.21).

Fig. 6

7. Represent the circuit using a Feedback Block diagram.

Solution:

8. Calculate the input resistance of the open loop and closed loop system and compare.

Solution:

For the cascaded system of $Q1$ and $Q2$, the input resistance of the system R_{in} ,

$$R_{in} = R_{inQ1} \quad (8.1)$$

To calculate the input resistance of the system, shot the independent sources and find the ratio

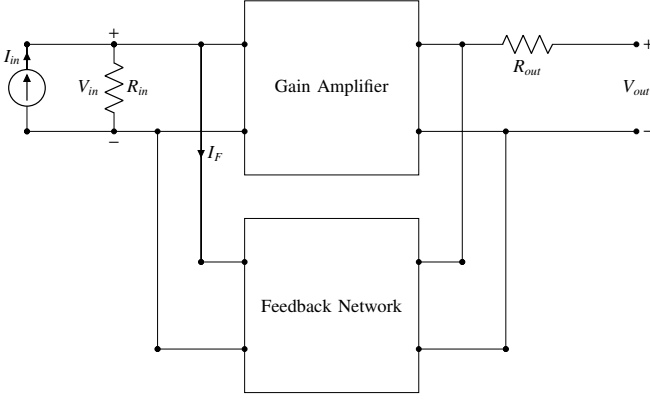


Fig. 7: Shunt-Shunt Feedback

$\frac{V_{in}}{I_{in}}$. As, $Q1$ is in common-emitter stage, from the fig. 1,

$$R_{in} = r_{\pi 1} \quad (8.2)$$

$$= 8130\Omega \quad (8.3)$$

After feedback is applied, to calculate input resistance, consider an input source V_{in} is connected to the input,

$$V_{out} = I_{in}G = \frac{V_{in}}{R_{in}}G \quad (8.4)$$

But as feedback is applied,

$$V_{in} = V_{out}H = \frac{V_{in}}{R_{in}}GH \quad (8.5)$$

Applying KVL for input loop in fig. 7,

$$\left(I_{in} - \frac{V_{in}}{R_{in}}GK\right)R_{in} = V_{in} \quad (8.6)$$

$$\Rightarrow R_{in_{cl}} = \frac{V_{in}}{I_{in}} = \frac{R_{in}}{1 + GH} \quad (8.7)$$

where, R_{in} is the input resistance of open loop. Therefore, R_{in} after feedback:

$$R_{in} = \frac{r_{\pi 1}}{1 + GH} \quad (8.8)$$

$$= \frac{8130}{10.95} = 742\Omega \quad (8.9)$$

The input should act as an ideal current source, so as the input resistance is decreased, the feedback gives more favourable value of R_{in} .

9. Calculate the output resistance of the open loop and closed loop system and compare.

Solution:

Similar to the input resistance, the output re-

sistance of the cascaded system is the output resistance of $Q2$. As $Q2$ is in emitter follower configuration, from the fig. 1,

$$R_{out} = \frac{1}{g_{m2}} \quad (9.1)$$

$$= \frac{1}{0.023} = 43.37\Omega \quad (9.2)$$

To calculate output resistance after feedback is applied, consider a voltage source V_X applied at V_{out} with output current I_X :

$$V_{in} = HV_X \quad (9.3)$$

$$\Rightarrow V_{out} = GHV_X \quad (9.4)$$

Applying KVL at output loop,

$$\frac{GHV_X + V_X}{R_{out}} = I_X \quad (9.5)$$

The closed loop output impedance,

$$R_{out_{cl}} = \frac{V_X}{I_X} \quad (9.6)$$

$$= \frac{R_{out}}{1 + GH} \quad (9.7)$$

The output resistance after feedback:

$$R_{out} = \frac{43.37}{10.95} = 3.96\Omega \quad (9.8)$$

The output should act as an ideal voltage source, i.e the output resistance should be as low as possible. As feedback reduces the values of R_{out} , it causes the output resistances to be more favourable.